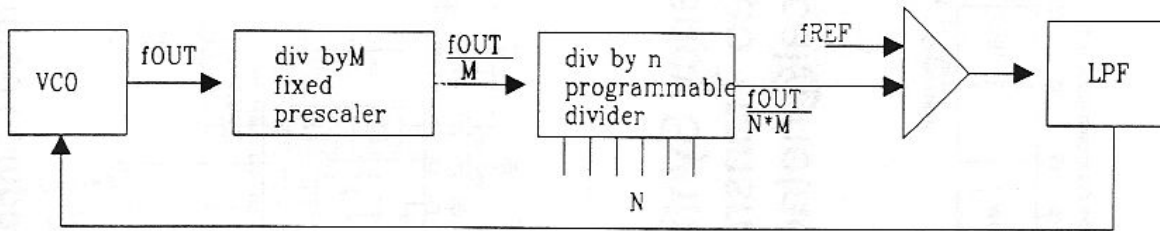


PLL Design

This is a preliminary design for a digitally synthesized fm stereo transmitter using the BA1404, MC145151-1(pll synthesizer) and the MC12019(div by 10/11 prescaler).



$$f_{IN} = f_{REF}$$

$$f_{IN} = \frac{f_{OUT}}{N \cdot M}$$

$$f_{OUT} = (N \cdot M) f_{REF}$$

$$f_{OUT} = N(M \cdot f_{REF}) \rightarrow f_{STEP} = M \cdot f_{REF}$$

We Want:

$$f_{STEP} = 100\text{kHz}$$

$$f_{OUT} = 87.5 - 108.1\text{MHz}$$


$$M = 20 \rightarrow \text{MC12019}$$

$$N = 3 - 16383 \rightarrow \text{MC145151-1}$$

$$f_{REF} = \frac{f_{STEP}}{M} = 5\text{kHz}$$

(5kHz * 1024)*2 = 10.24 mhz Ref Osc. for MC145151-1
using 100 for the reference address divide value
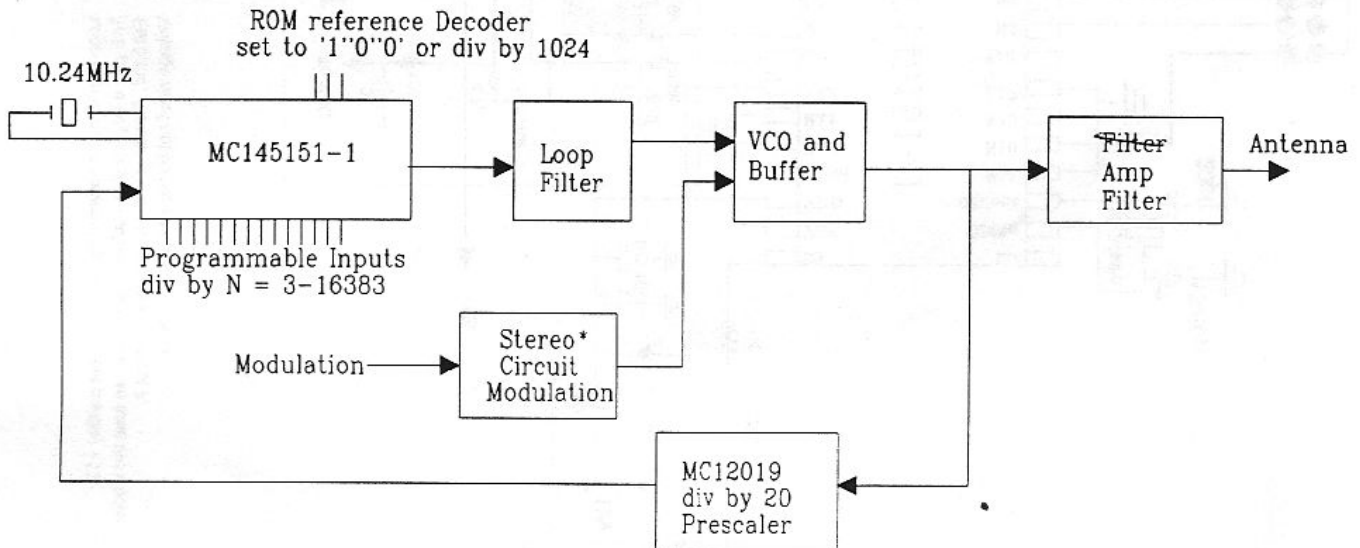
$$N = \frac{f_{OUT}(\text{mhz})}{f_{REF}} \rightarrow \text{so } 87.5\text{mhz} \rightarrow n=875, 108.1\text{mhz} \rightarrow n=1081... \text{ totally cool}$$



* Stereo Modulation Circuit - See notes under car CD player

o We are only interested in N=877 to 1081 we can limit the inputs to this range or be careful not to go out of these bounds.

o I am having trouble finding examples on how to modulate the VCO, most PLL books have this block diagram but give no circuit examples.

o The filter-amp-filter section will be close to simple 3 element filter from the FM-10 FAQ, an amp close to the dual 901 amp, and another 3 element filter. I am hoping for between 100mw-500mw, depending on the output from the VCO.

o Please see National Semiconductor "Interface Databook" 1990 for further info on PLL design, including schematics for VCO.

o Contact me for further info/spec sheets etc if you are project or have any ideas or examples for the above.